

$$V = V_+ e^{-\gamma l} + V_- e^{\gamma l}$$

$$I = I_+ e^{-\gamma l} - I_- e^{\gamma l}$$

$$T = \frac{V_{tr}}{V_{inc}} = \frac{V_+ e^{-\gamma l}}{V_+ e^{-\gamma l} + V_- e^{\gamma l}}$$

$$= \frac{I_+ e^{-\gamma l} - V_- e^{\gamma l}}{V_+ e^{-\gamma l}}$$

$$= \frac{I_{tr}}{I_{inc}}$$

$$V_{tr} e^{-\gamma l} = V_+ e^{-\gamma l} + V_- e^{\gamma l}$$

$$I = \frac{1}{Z_0} (V_+ e^{-\gamma l} - V_- e^{\gamma l})$$

$$I_{tr} e^{-\gamma l} = \frac{1}{Z_0} (V_+ e^{-\gamma l} - V_- e^{\gamma l})$$

$$\frac{V_{tr}}{Z_e} e^{-\gamma l} = \frac{1}{Z_0} (V_+ e^{-\gamma l} - V_- e^{\gamma l})$$

$$\frac{V_+ e^{-\gamma l}}{Z_0 + Z_e}$$

$$T = \frac{2Z_e}{Z_0 + Z_e}$$

In a transmission line,  $Z_0 =$

$$\& Z_L = 70 + j50 \Omega \quad 75 + j0.01 \Omega$$

- i) reflection coefficient
- ii) transmission coefficient
- iii) Verify relation between  $\Gamma$  &  $T$

~~NO~~

~~145~~

i)

$$75 + j0.01 - 70 - j50$$

$$\hline 145 + j50.01$$

$$= -5 + j49.99$$

$$\hline 145 + j50.01$$

$$= \frac{220}{20 + 20}$$

$$\hline 20 + 20$$

$$150 + j0.02$$

$$\hline 145 + j50.01$$

$$T = (1 + \Gamma)$$

or

$$\Gamma = \frac{Z_0 - Z_L}{Z_0 + Z_L} Z_0$$

$$T = \frac{2Z_0}{Z_0 + Z_L}$$

$$T = \frac{Z_0 + Z_L + Z_0 - Z_L}{Z_0 + Z_L}$$

$$= 1 + \Gamma$$

$$\begin{aligned} & (145)^2 + \\ & (50.01)^2 \\ & = \end{aligned}$$

$$\begin{aligned} & 21025 + \cancel{2501.00} \\ & 2501.0001 \end{aligned}$$

$$\begin{aligned} & - (23526.0001) \\ & \frac{(-5 + 49.999)}{(23526.0001)} (145 \pm 50.021) \end{aligned}$$

# $Z_L^2$ Standing Wave ( $V_s$ )




$$V = V_+ e^{-\gamma z} + V_- e^{\gamma z}$$

(Voltage expression of  $T_x$ )

$$\gamma = \alpha + j\beta$$

$$\begin{aligned} & V_+ e^{-(\alpha - j\beta)z} + V_- e^{(\alpha + j\beta)z} \\ &= V_+ e^{-\alpha z - j\beta z} + V_- e^{\alpha z + j\beta z} \end{aligned}$$
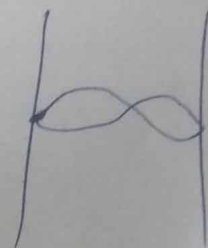
$$\begin{aligned} \text{Let } V_+ e^{-\alpha z} &= A \\ V_- e^{\alpha z} &= B \end{aligned}$$



$$V_+ e^{-\alpha z}$$

$$V_+ \sin(\cos \beta z - j \sin \beta z)$$

$$+ V_- (\cos \beta z + j \sin \beta z)$$

$$= V_+ \cos \beta z$$

$$\frac{(V_+ + V_-) \cos \beta z + j(V_+ - V_-) \sin \beta z}{\sin \beta z}$$



$$= A[\cos \beta z - j \sin \beta z] + B[\cos \beta z + j \sin \beta z]$$

$$= \sqrt{(A+B)^2 \cos^2 \beta z + (A-B)^2 \sin^2 \beta z}$$

$$V_S = V_S = V_0 e^{-j\phi}$$

$$\text{So } \phi = \beta z$$

~~$V_0$~~

$$A+B$$

$$\cancel{A+B}$$

$$\phi = \tan^{-1} \left( \frac{(A-B) \sin \beta z}{(A+B) \cos \beta z} \right)$$

$$\Rightarrow \phi = \tan^{-1} \left( \frac{A-B}{A+B} \tan \beta z \right)$$

$$\text{or } \arctan \left( \frac{b}{a} \right)$$

$$= \tan^{-1} \left( \frac{V_+ e^{-\alpha z} - V_- e^{\alpha z}}{V_+ e^{-\alpha z} + V_- e^{\alpha z}} \tan \beta z \right)$$

$$\cos a \cos b + \sin a \sin b = \cos(a-b)$$

$$\cancel{\sin a \cos b}$$

$$a \cos b + b \sin b$$

✓

$$\sqrt{A^2 + B^2 + 2AB(\cos^2 \beta^2 - \sin^2 \beta^2)}$$

$$= \sqrt{A^2 + B^2 + 2AB \cos 2\beta^2}$$

$$A + B$$

$$\frac{dV_0}{d\beta}$$

$$\frac{d}{dz}$$

$$- \frac{2}{\cancel{A}} AB \sin 2\beta^2$$

$$\cancel{\sqrt{A^2 + B^2 + 2AB \cos 2\beta^2}} \quad \therefore$$

$$= -2AB \sin 2\beta^2$$

$$V_{max} = V_+ e^{-\alpha z} + V_- e^{\alpha z}$$

$$= V_+ e^{-\alpha z} (1 + |\Gamma|)$$

$$V_{min} = V_+ e^{-\alpha z} - V_- e^{\alpha z}$$

$$= V_+ e^{-\alpha z} (1 - |\Gamma|)$$

$$\frac{V_{SWR}}{V_{min}}$$

Voltage standing wave  
ratio

$$= \frac{|V_{max}|}{|V_{min}|}$$

$$= \frac{|1 + \Gamma|}{|1 - \Gamma|}$$

S	A	B	C <sub>in</sub>
0	0	0	0
0	0	0	0

$$\begin{aligned} &BC_{in} \\ &+ AC_{in} \\ &+ AB \end{aligned}$$


---


$$\bar{A} \bar{B} C$$



Cyber: Relating or Characteristics of the culture of

# Line Impedance of Transmission Line

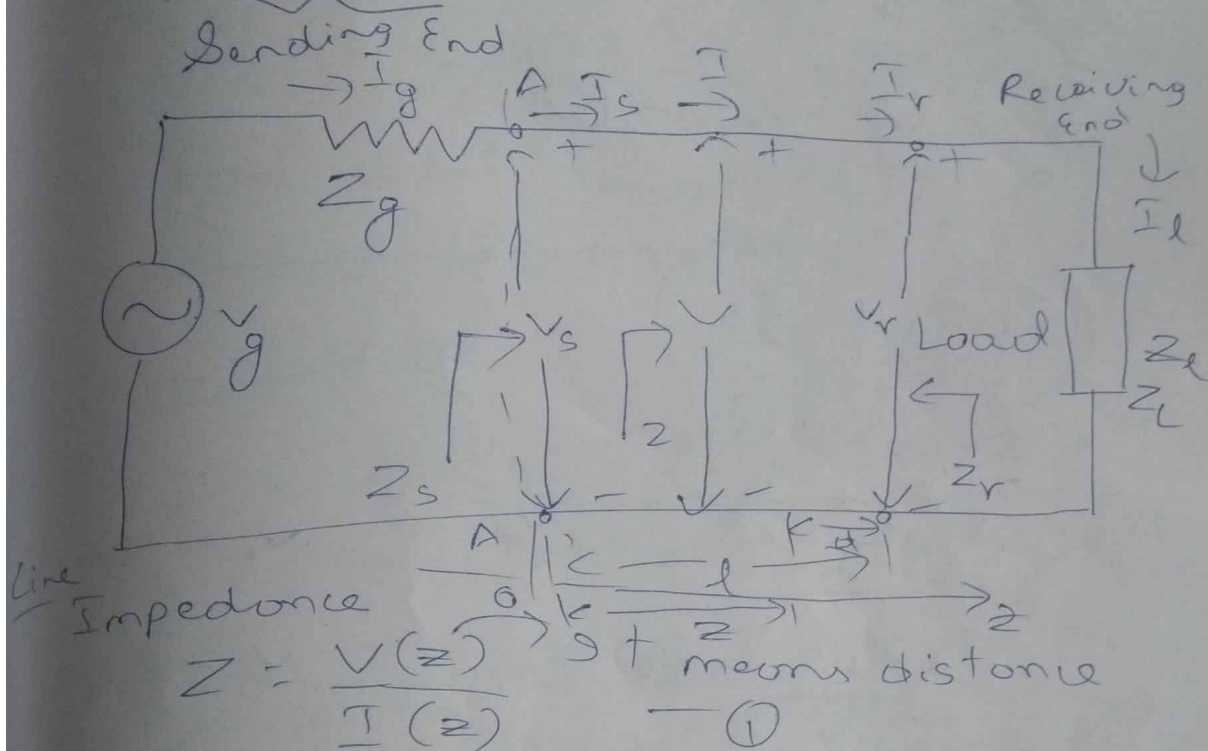

$$V = V_{inc}$$

$$V = V_+ e^{-\gamma z} + V_- e^{+\gamma z} \quad \text{--- (2)}$$

$$I = \frac{V}{Z_0} + \frac{1}{Z_0} (V_+ e^{-\gamma z} - V_- e^{+\gamma z}) \quad \text{--- (3)}$$

$$= Y_0 (V_+ e^{-\gamma z} - V_- e^{+\gamma z})$$

Character  
Characteristic  
Admittance

At source,  $z=0$

$$V_s = V_+ + V_- \quad V_s = I_s Z_s = V_+ + V_-$$

$$I_s = Y_0 (V_+ - V_-) \quad I_s = Y_0 (V_+ - V_-)$$

~~7~~

$$V_+ + V_- = V_S$$

$$V_+ - V_- = \frac{I_S}{Y_0} Z_S$$

$$I_S Z_S = V_+ + V_- \quad (4)$$

$$\frac{I_S}{Y_0} = V_+ - V_- \quad (5)$$

$$\left( \frac{I_S Z_S}{2} + \frac{I_S}{2 Y_0} \right)$$

$$\frac{I_S Z_S + \frac{I_S}{Y_0} Z_0}{2} = V_+$$

$$\frac{I_S Z_S - \frac{I_S}{Y_0} Z_0}{2} = V_-$$

$$V_+ = \frac{I_S}{2} (Z_S + Z_0) \quad (6)$$

$$V_- = \frac{I_S}{2} (Z_S - Z_0) \quad (7)$$

$$\frac{V_S + I_S Z_0}{2} = V_+$$

$$\frac{V_S - I_S Z_0}{2} = V_-$$

$$V_g = \frac{I_S}{2} (Z_S + Z_0) e^{-\gamma z} + \frac{I_S}{2} (Z_S - Z_0) e^{+\gamma z}$$

$$I = \frac{1}{Z_0} \frac{I_S}{2} \left( (Z_S + Z_0) e^{-\gamma z} - (Z_S - Z_0) e^{+\gamma z} \right)$$

So line impedance in terms of source and is

$$= \frac{(Z_s + Z_0)e^{-\gamma z} + (Z_s - Z_0)e^{\gamma z}}{(Z_s + Z_0)e^{-\gamma z} - (Z_s - Z_0)e^{\gamma z}} Z_0$$

$$V = V_+ e^{-\gamma z} + V_- e^{\gamma z}$$

$$I = \frac{1}{Z_0} (Z V_+ e^{-\gamma z} - V_- e^{\gamma z})$$

for total length (l),

~~$$Z = Z_0 \frac{(Z_s + Z_0)e^{-\gamma l} + (Z_s - Z_0)e^{\gamma l}}{(Z_s + Z_0)e^{-\gamma l} - (Z_s - Z_0)e^{\gamma l}}$$~~

~~$$Z = Z_0 (Z_s + Z_0)$$~~

$$Z = Z_0 \frac{(Z_s + Z_0)e^{-\gamma l} + (Z_s - Z_0)e^{\gamma l}}{(Z_s + Z_0)e^{-\gamma l} - (Z_s - Z_0)e^{\gamma l}}$$

At any point  $z = d$

$$Z = Z_0 \frac{(Z_s + Z_0)e^{-\gamma(l-d)} + (Z_s - Z_0)e^{\gamma(l-d)}}{(Z_s + Z_0)e^{-\gamma(l-d)} - (Z_s - Z_0)e^{\gamma(l-d)}}$$

$$Z = Z_0 \frac{Z_s}{Z_0}$$


$$= Z_s$$

Virus is on active  
malware software  
& worm is also  
that.

At  
Normalized impedance (It looks like relative refractive index)

It is ratio of  
 simple impedance by  
 characteristic impedance
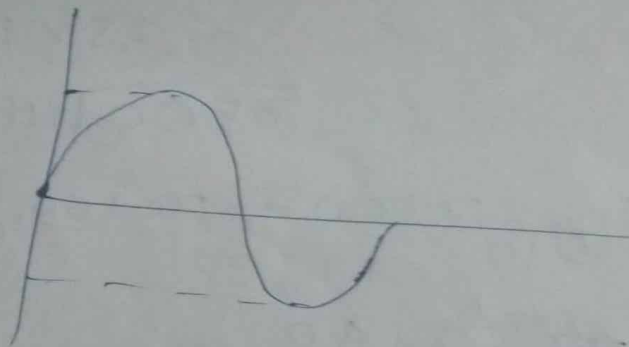
$$\text{So, } Z = \frac{Z}{Z_0} = \frac{1 + \Gamma}{1 - \Gamma}$$



$$Z_{\max} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

$$Z_{\min} = \frac{1 - |\Gamma|}{1 + |\Gamma|}$$

$$= \frac{1}{f \text{ VSWR}}$$

This is got  
 by the above  
 sine wave.

For max,

$$\Gamma > 0$$

for min

$$\Gamma < 0$$

## Smith Chart

$$\Gamma_l = \frac{Z_l - Z_0}{Z_l + Z_0}$$

~~$$\Gamma_d = \Gamma_l e^{-j2\alpha d}$$~~

$$\Gamma_d = \Gamma_l e^{j2\gamma d}$$

$$= \Gamma_l e^{j2(\alpha + j\beta)d}$$

to follow graph