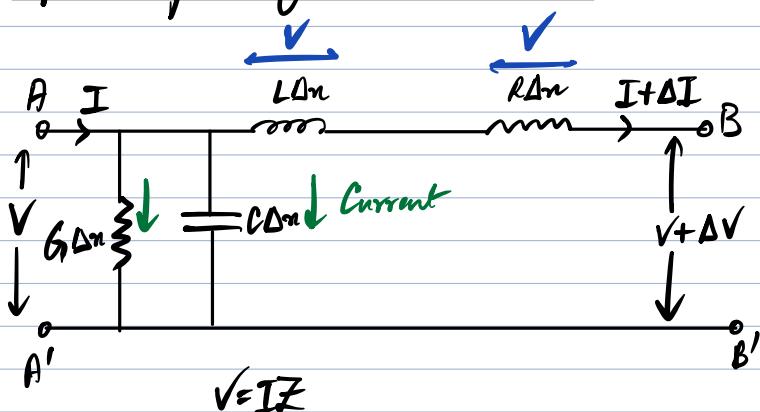


All possible combinations are possible.

- i) C (Parallel) $\rightarrow \text{---}$
 - ii) R (Series) $\rightarrow \text{---}$
 - iii) L (Series) $\rightarrow \text{---}$
 - iv) G (Parallel) $\rightarrow \text{---}$
- 'Primary Constants of the line'

Equations of Voltage and Current



$$\left\{ \begin{array}{l} \Delta V = -(R\Delta x + j\omega L\Delta x)I \\ \Delta I = -(G\Delta x + j\omega C\Delta x)V \end{array} \right. \quad \begin{array}{l} \textcircled{1} \\ \textcircled{2} \end{array}$$

$$\left\{ \begin{array}{l} \frac{\Delta V}{\Delta x} = -(R + j\omega L)I \\ \frac{\Delta I}{\Delta x} = -(G + j\omega C)V \end{array} \right. \quad \left| \begin{array}{l} \textcircled{3} \\ \textcircled{4} \end{array} \right| \quad \left| \begin{array}{l} \because \Delta x \rightarrow 0 \Rightarrow \frac{\Delta V}{\Delta x} = \frac{dV}{dx} \\ \frac{\Delta I}{\Delta x} = \frac{dI}{dx} \end{array} \right.$$

$$\left\{ \begin{array}{l} \frac{dV}{dx} = -(R + j\omega L)I \\ \frac{dI}{dx} = -(G + j\omega C)V \end{array} \right. \quad \left| \begin{array}{l} \textcircled{5} \\ \textcircled{6} \end{array} \right| \quad \left| \begin{array}{l} \textcircled{7} \\ \textcircled{8} \end{array} \right|$$

$$\frac{d^2V}{dx^2} = -(R + j\omega L) \frac{dI}{dx}$$

$$\Rightarrow \frac{d^2V}{dx^2} = (R + j\omega L)(G + j\omega C)V$$

$$\frac{d^2V}{dx^2} = \gamma^2 V$$

$\gamma \rightarrow$ Propagation Constant

Similarly, $\frac{d^2I}{dx^2} = \gamma^2 I$

(10)

(9) & (10) \rightarrow Homogeneous eqns. with constant coeff.

$$V = V^+ e^{-\gamma x} + V^- e^{\gamma x} \quad (12)$$

$$I = I^+ e^{-\gamma x} + I^- e^{\gamma x} \quad (13)$$

$$V(t) = (V^+ e^{-\gamma x} + V^- e^{\gamma x}) e^{j\omega t}$$

$$\Rightarrow V(t) = (V^+ e^{-\gamma x + j\omega t} + V^- e^{\gamma x + j\omega t})$$

$$I(t) = (I^+ e^{-\gamma x + j\omega t} + I^- e^{\gamma x + j\omega t})$$

$$\because \gamma \text{ is a complex no. so } \underline{\gamma} = \alpha + j\beta$$

$$V(t) = (V^+ e^{-(\alpha+j\beta)x + j\omega t} + V^- e^{(\alpha+j\beta)x + j\omega t})$$

$$\Rightarrow V(t) = [V^+ e^{-\alpha x} e^{j(-\beta x + \omega t)} + V^- e^{\alpha x} e^{j(\beta x + \omega t)}] \quad (16)$$

$$\times I(t) = [I^+ e^{-\alpha x} e^{j(-\beta x + \omega t)} + I^- e^{\alpha x} e^{j(\beta x + \omega t)}] \quad (17)$$

$\alpha \rightarrow$ Attenuation const.

$\beta \rightarrow$ Phase const.

$$\beta = \frac{2\pi}{\lambda}$$

L	dist
$2\pi \rightarrow \lambda$	
$\lambda \rightarrow 2\pi$	
$\beta = 2\pi/\lambda$	

$$V^+ e^{-\alpha x} \rightarrow (+) ve n \text{ dim.}$$



$$\frac{dV}{dx} = -(R + j\omega L)I \quad (5)$$

$$\frac{dI}{dx} = -(G + j\omega C)V \quad (6)$$

$$V = V^+ e^{-\gamma x} + V^- e^{\gamma x} \quad (12)$$

$$I = I^+ e^{-\gamma x} + I^- e^{\gamma x} \quad (13)$$

$$\frac{d}{dx} (V^+ e^{-\gamma x} + V^- e^{\gamma x}) = -(R + j\omega L) (I^+ e^{-\gamma x} + I^- e^{\gamma x})$$

$$\Rightarrow -\gamma V^+ e^{-\gamma x} + \gamma V^- e^{\gamma x} = -(R + j\omega L) I^+ e^{-\gamma x} - (R + j\omega L) I^- e^{\gamma x}$$

$$e^{-\gamma x}$$

$$-\gamma V^+ e^{-\gamma x} = -(R + j\omega L) I^+ e^{-\gamma x}$$

$$\Rightarrow \frac{V^+}{I^+} = \frac{(R + j\omega L)}{\gamma} = Z_0$$

$$\Rightarrow Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$e^{\gamma x}$$

$$\gamma V^- e^{\gamma x} = -(R + j\omega L) I^- e^{\gamma x}$$

$$\Rightarrow \frac{V^-}{I^-} = \frac{-(R + j\omega L)}{\gamma} = -Z_0$$

$$\Rightarrow \frac{V^-}{I^-} = -Z_0 = -\sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$\gamma^2 = (G + j\omega C)(R + j\omega L) \Rightarrow \gamma = \sqrt{(G + j\omega C)(R + j\omega L)}$$

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$


Characteristic Impedance

$$\boxed{\frac{V^+}{I^+} = Z_0 \quad \& \quad \frac{V^-}{I^-} = -Z_0} \rightarrow I^+ = \frac{V^+}{Z_0} \quad \& \quad I^- = \frac{-V^-}{Z_0}$$

Now, $\left\{ \begin{array}{l} V = V^+ e^{-\gamma x} + V^- e^{\gamma x} \\ I = I^+ e^{-\gamma x} + I^- e^{\gamma x} \end{array} \right. \quad (27)$
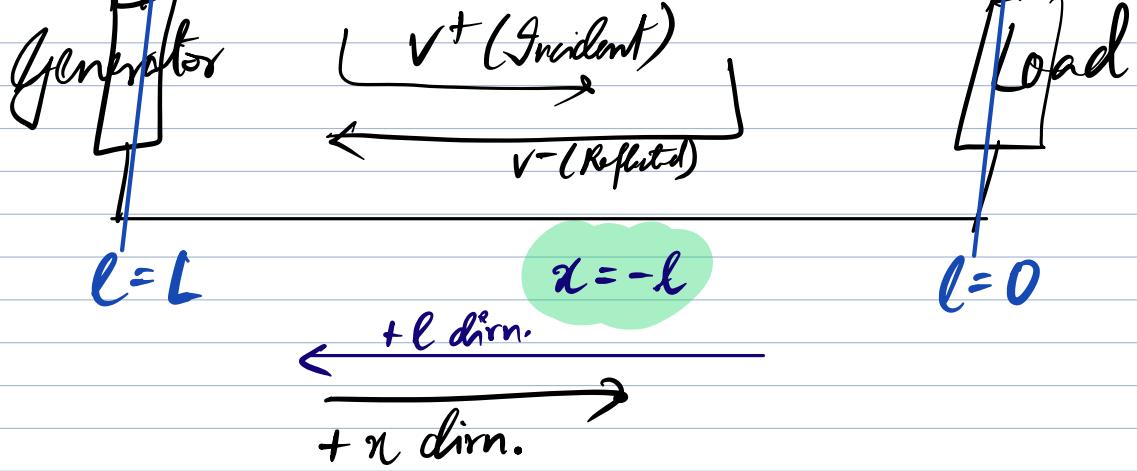
$$I = I^+ e^{-\gamma x} + I^- e^{\gamma x} = \frac{V^+}{Z_0} e^{-\gamma x} - \frac{V^-}{Z_0} e^{\gamma x} \quad (28)$$





$$V(l) = V^+ e^{j\delta l} + V^- e^{-j\delta l} \quad (29)$$

$$I(l) = I^+ e^{j\delta l} + I^- e^{-j\delta l} \quad (30)$$

Reflection Coefficient, $\Gamma(l) = \frac{V^- e^{-j\delta l}}{V^+ e^{j\delta l}} = \left(\frac{V^-}{V^+}\right) e^{-2j\delta l}$ — (31)

$$V(l) = V^+ e^{j\delta l} \left[1 + \frac{V^- e^{-j\delta l}}{V^+ e^{j\delta l}} \right]$$

$$V(l) = V^+ e^{j\delta l} (1 + \Gamma(l))$$

$$I(l) = \frac{V^+}{Z_0} e^{j\delta l} - \frac{V^-}{Z_0} e^{-j\delta l} = \frac{V^+}{Z_0} e^{j\delta l} \left[1 - \frac{V^- e^{-j\delta l}}{V^+ e^{j\delta l}} \right]$$

$$I(l) = \frac{V^+}{Z_0} e^{j\delta l} [1 - \Gamma(l)]$$

$$V(l) = V^+ e^{j\delta l} (1 + \rho(l)) \quad (32)$$

$$I(l) = \frac{V^+}{Z_0} e^{j\delta l} (1 - \Gamma(l)) \quad (33)$$

$$Z(l) = \frac{V(l)}{I(l)} = Z_0 \left(\frac{1 + p(l)}{1 - p(l)} \right)$$

Impedance at any point 'l' on the Tx line starting from the load end.

Mathematics yields

$$p(l) = \frac{Z(l) - Z_0}{Z(l) + Z_0}$$

Reflection Coeff. at any fl. 'l'

$$l=0 \rightarrow \text{load end} \rightarrow p(l=0) \equiv P_L$$

$$p(l=0) = P_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$p(l) = \left(\frac{\sqrt{+}}{\sqrt{+}} e^{-j\ell} \right) \Rightarrow P_L = p(l=0) = \frac{\sqrt{-}}{\sqrt{+}}$$

$$\Rightarrow P(l) = P_L e^{-j\ell} = P_L e^{-2\pi l}$$

$$V(l) = V^+ e^{j\ell} [1 + p(l)]$$

$$\Rightarrow V(l) = V^+ e^{j\ell} [1 + P_L e^{-2\pi l}]$$

$$I(l) = \frac{V^+}{Z_0} e^{j\ell} [1 - p(l)]$$

$$= \frac{V^+}{Z_0} e^{j\ell} [1 - P_L e^{-2\pi l}]$$

$$\Rightarrow Z(l) = Z_0 \left[\frac{1 + P_L e^{-2\pi l}}{1 - P_L e^{-2\pi l}} \right] \left(\frac{V^+ e^{j\ell}}{I(l)} \right)$$

Impedance Transformation Equation

$$Z(l) = Z_0 \left[\frac{Z_L \cosh j\ell + Z_0 \sinh j\ell}{Z_L \sinh j\ell + Z_0 \cosh j\ell} \right]$$

$$\text{Reflection Coefficient, } \Gamma(l) = \frac{V^- e^{-\gamma l}}{V^+ e^{\gamma l}} = \left(\frac{V^-}{V^+}\right) e^{-2\gamma l} \quad \text{--- (21)}$$

$$\Gamma(l) = \frac{Z(l) - Z_0}{Z(l) + Z_0} \quad \text{--- (22)}$$

Reflection Coeff. at $l=0$ (i.e. load end), $\Gamma(0) = \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$

$$T = 1 + \Gamma$$

Transmission Coefficient, $T = \frac{2Z_L}{Z_L + Z_0}$

$Z_L \rightarrow \text{load Impedance}$

$Z_0 \rightarrow \text{Characteristic Impedance}$

Transmission Lines

23

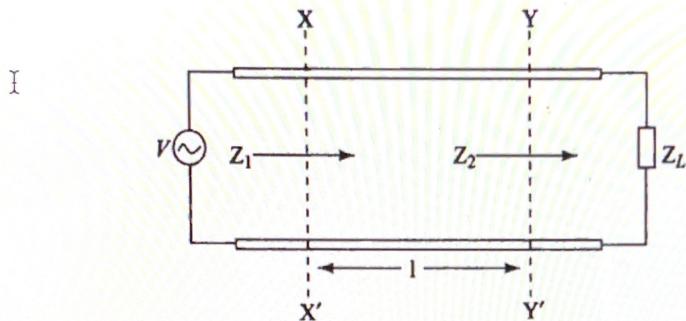


Fig. 2.8 Impedance transformation on a transmission line.

It should be noted here that although Eqn (2.45) gives the transformation of the load impedance, there is nothing special about the load impedance. We obtained transformation of load impedance because we defined $l = 0$ at the load end. If we define $l = 0$ at some other location on the line we get transformation of the impedance from that point. We can therefore generalise the impedance transformation equation for any two points on the transmission line.

Let the impedances measured at two locations on the line be Z_1 and Z_2 respectively as shown in Fig. 2.8.

Then from Eqn (2.45) we get

$$Z_1 = Z_0 \left[\frac{Z_2 \cosh \gamma l + Z_0 \sinh \gamma l}{Z_2 \sinh \gamma l + Z_0 \cosh \gamma l} \right] \quad (2.46)$$

If we invert Eqn (2.46) we get

$$Z_2 = Z_0 \left[\frac{Z_1 \cosh \gamma l - Z_0 \sinh \gamma l}{-Z_1 \sinh \gamma l + Z_0 \cosh \gamma l} \right] \quad (2.47)$$

Since, $\sinh(-\gamma l) = -\sinh \gamma l$ and $\cosh(-\gamma l) = \cosh \gamma l$, Eqn (2.47) can be re-written as

$$Z_2 = Z_0 \left[\frac{Z_1 \cosh(-\gamma l) + Z_0 \sinh(-\gamma l)}{Z_1 \sinh(-\gamma l) + Z_0 \cosh(-\gamma l)} \right] \quad (2.48)$$

From Eqns (2.46) and (2.48) it is evident that the two expressions are identical

Loss-Less And Low-Dissipation Transmission Lines

We know, propagation constant, $\gamma = \sqrt{(R+j\omega L)(G+j\omega C)}$

and characteristic impedance, $Z_0 = \sqrt{\frac{R+j\omega L}{G+j\omega C}}$

For Loss-Less Tx line \Rightarrow No Resistance & Conductance
So, $R=0$ & $G=0$

$$\text{i) } \gamma = \sqrt{(j\omega L)(j\omega C)} = j\omega\sqrt{LC}$$

$$\text{ii) } Z_0 = \sqrt{\frac{j\omega L}{j\omega C}} = \sqrt{\frac{L}{C}}$$

Characteristics of loss-less

$$\text{i) } Z(l+\lambda/2) = Z(l)$$

$$\text{ii) } \bar{Z}(l+\omega/4) = \frac{1}{\bar{Z}(l)}$$

$$\text{iii) If } Z_L = Z_0 \Rightarrow Z(l) = Z_0$$

For low-dissipation Transmission line

$$\begin{aligned} \gamma &= \alpha + j\beta = \sqrt{(R+j\omega L)(G+j\omega C)} \\ &= \sqrt{j\omega L \left\{ 1 - j\frac{R}{\omega L} \right\} j\omega C \left\{ 1 - j\frac{G}{\omega C} \right\}} \end{aligned}$$

$$\gamma = \alpha + j\beta = j\omega\sqrt{LC} \left\{ 1 - j\frac{R}{2\omega L} \right\} \left\{ 1 - j\frac{G}{2\omega C} \right\}$$

On further simplification

$$\gamma = \alpha + j\beta = j\omega\sqrt{LC} \left\{ 1 - j\frac{R}{2\omega L} - j\frac{G}{2\omega C} \right\}$$

So, $\alpha = \frac{R}{2\sqrt{LC}} + \frac{G}{2\sqrt{LC}}$

for low-dissipation Tx line

$$\beta = \omega\sqrt{LC}$$

Voltage Standing Wave Ratio (VSWR)

Now, $V(l) = V^+ e^{j\ell} (1 + \rho(l))$

$$I(l) = \frac{V^+ e^{j\ell}}{Z_0} (1 - \rho(l))$$

$$\text{and } \rho(l) = \frac{V^-}{V^+} e^{-2jl} = \frac{Z(l) - Z_0}{Z(l) + Z_0}$$

$$\therefore \rho(l) = \rho_L e^{-2jl}$$

Now, $\rho_L = \rho(0) = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{V^-}{V^+}$

$$\therefore V(l) = V^+ e^{j\ell} (1 + \rho_L e^{-2jl})$$

$$\begin{aligned} \rightarrow |V|_{\max} &= |V^+| / (1 + |\rho_L|) \\ \rightarrow |V|_{\min} &= |V^+| / (1 - |\rho_L|) \end{aligned}$$

$$I(l) = \frac{V^+}{Z_0} e^{j\ell} (1 - \rho_L e^{-2jl})$$

$$\begin{aligned} \rightarrow |I|_{\max} &= \left| \frac{V^+}{Z_0} \right| (1 + |\rho_L|) = \frac{|V|_{\max}}{Z_0} \\ \rightarrow |I|_{\min} &= \left| \frac{V^+}{Z_0} \right| (1 - |\rho_L|) = \frac{|V|_{\min}}{Z_0} \end{aligned}$$

Voltage Standing Wave Ratio (VSWR), $f = \frac{|V|_{\max}}{|V|_{\min}}$ (f is always $> 1 \because |V|_{\max} > |V|_{\min}$)

$$\Rightarrow f = \frac{1 + |\rho_L|}{1 - |\rho_L|} \quad \begin{aligned} \text{when } |\rho_L| = 0 &\Rightarrow f = 1 \\ \text{when } |\rho_L| = 1 &\Rightarrow f = \infty \end{aligned}$$

$$\Rightarrow |\rho_L| = \frac{f-1}{f+1}$$

Power Transfer of a Transmission line, $P_L = \frac{|V|^2}{2Z_0} \{1 - |\rho_L|^2\}$