

Microwave Integrated Circuits (OE-EC 804 B)  
 Frequency range  $300 \text{ MHz}$  to  $300 \text{ GHz}$

$$E = h\nu = h \frac{c}{\lambda}$$


$$\text{Frequency} = \frac{c}{\lambda} \times 100$$

$$3 \times 10^6 = 3 \times 10^8$$


$$\lambda = 100 \text{ m}$$

$$3 \times 10^9 \times 100 = 3 \times 10^8$$
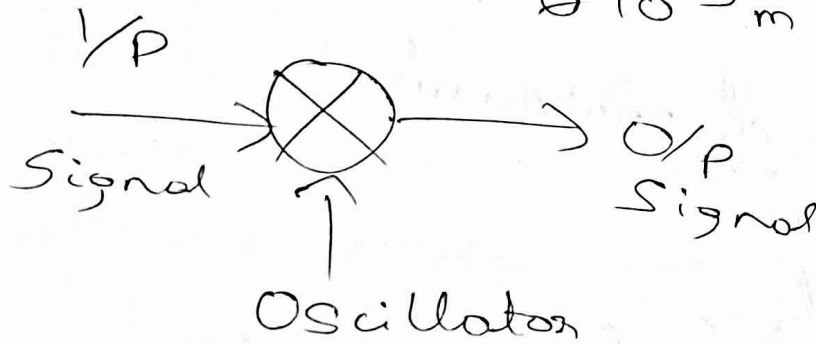
$$\Rightarrow \lambda = 10^{-3} \text{ m}$$



$$R = \rho \frac{l}{A}$$

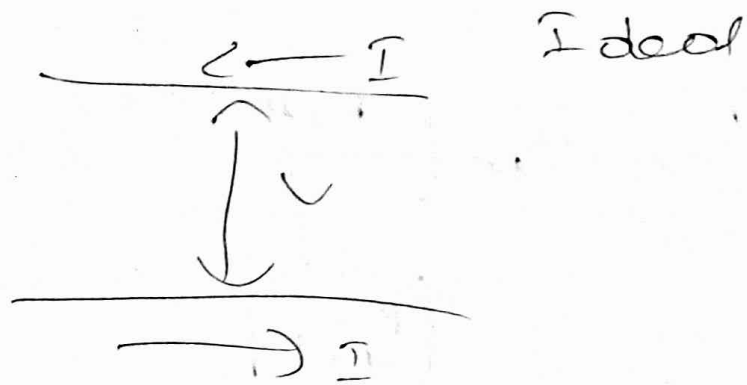

$$V = IR \rightarrow R = \frac{V}{I}$$

$$X = R + j\omega L + \frac{1}{j\omega C}$$


## MESFET

because of metal semiconductor contact, on applying small voltage, we get high current.

pic


# Microwave Transmission Lines

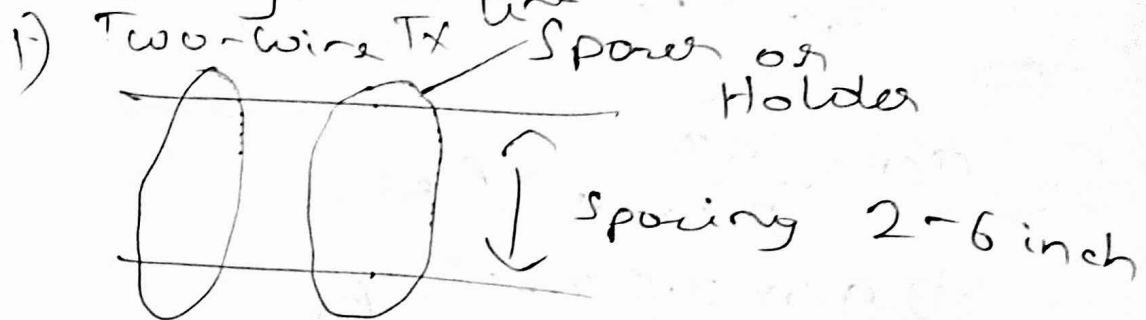- 1) Two-Wire Parallel T.L.
- 2) Co-axial Cable
- 3) Strip line
- 4) Waveguide




Disadvantage

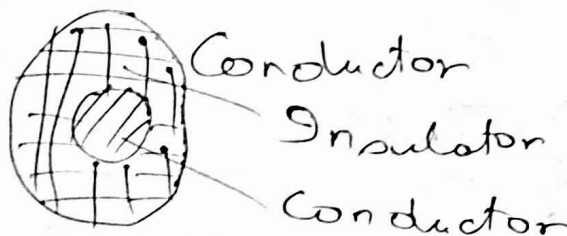- 1) Loss of energy is high.
- 2) Co-axial Cable




3) Strip-line

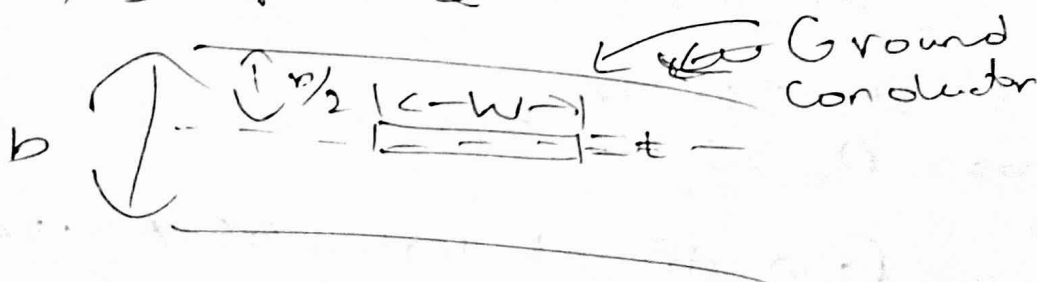


Ground should be minimum  
5 times greater than  $b$ .


Disadvantage

- i) It is inside dielectrics, so its <sup>position</sup> ~~can~~ be changed ~~in orientation~~ to when required.

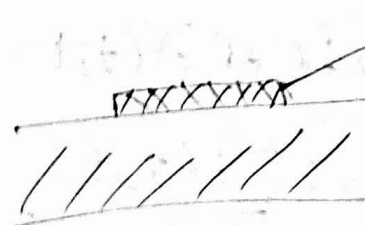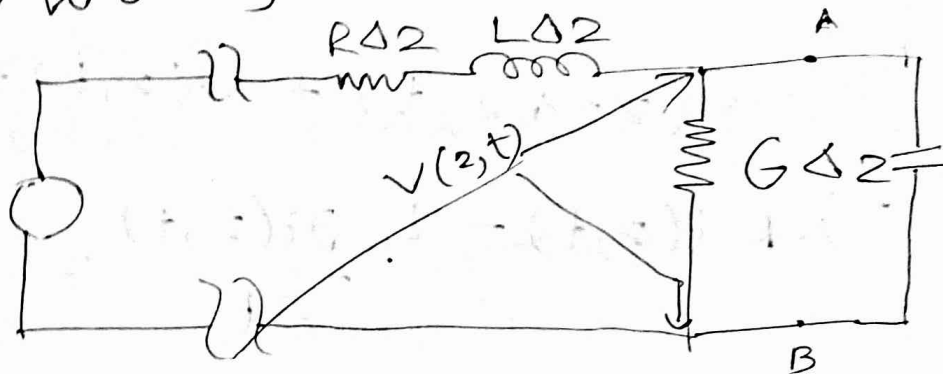
  
 $n$ -strip  
 // // // // - Insulator on  
 1) Waveguide



→ z

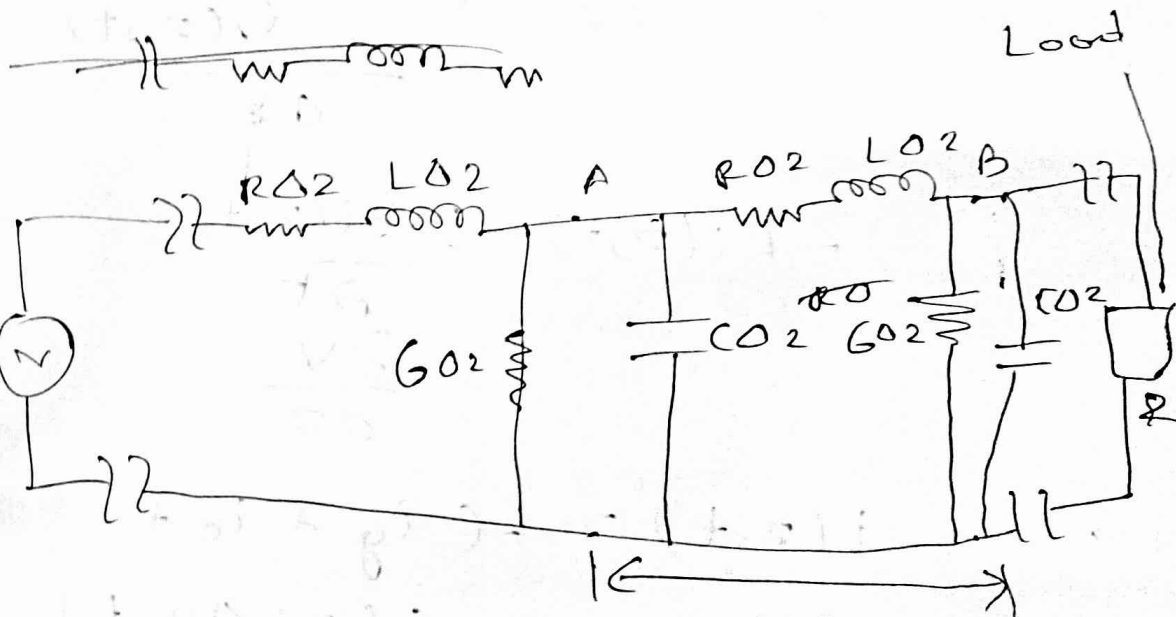

$(z, t)$

$$-i(z)R\Delta z - L\Delta z \frac{\partial i(z,t)}{\partial t}$$

$$v(z+\Delta z, t) +$$

$$v(z, t) = 0$$

$$v(z+\Delta z, t) - v(z, t)$$

$$\frac{\quad}{\Delta z} = -i(z,t)R - L\frac{\partial i(z,t)}{\partial t}$$

$$-R \Delta z i(z, t) - L \Delta z i \frac{\partial i(z, t)}{\partial t}$$

$$v(z + \Delta z, t) + v(z, t) = 0$$

$$\Rightarrow -R i(z, t) - L \frac{\partial i(z, t)}{\partial t} =$$

$$\frac{\partial v}{\partial z}$$

$$\frac{v(z + \Delta z, t) - v(z, t)}{\Delta z}$$

$$\Rightarrow -R i(z, t) - L \frac{\partial i(z, t)}{\partial t} =$$

$$\frac{\partial v}{\partial z}$$

$$i(z, t) = i_g + i_c +$$

$$i(z + \Delta z, t)$$

$$\Rightarrow -i_g - i_c = i(z + \Delta z, t) - i(z, t)$$

$$\Rightarrow -v(z + \Delta z, t) \Delta z =$$

$$\frac{\partial v(z + \Delta z, t)}{\partial t} \Delta z = i(z + \Delta z, t) - i(z, t)$$

$$\Rightarrow$$

$$\Rightarrow -V(z+\Delta z, t) \Delta z -$$

$$\frac{\partial V(z+\Delta z, t)}{\partial t} \Delta z = \frac{\partial i(z, t)}{\partial z} \Delta z$$

$$\cancel{V(z)} -$$

$$V(z, t) - R(\Delta z) R \Delta z \frac{\partial i(z, t)}{\partial t} =$$

$$\cancel{L \Delta z \partial i}$$

$$R \Delta z i(z, t) -$$

$$L \Delta z \frac{\partial i(z, t)}{\partial t} =$$

$$V(z+\Delta z, t)$$

## Characteristic Impedance

$$\frac{dv}{dz} = -Z I \quad \text{--- (1)}$$

$$V = V^+ e^{-\gamma z} + V^- e^{+\gamma z}$$

$$I = -\frac{1}{Z} \frac{dv}{dz}$$

$$\frac{dI}{dz} = -\frac{1}{Z^2} \frac{d^2 V}{dz^2}$$

$$\frac{dI}{dz} = +\frac{1}{Z^2} \frac{dv}{dz} - \frac{1}{Z} \frac{d^2 V}{dz^2}$$

$$= \frac{1}{Z} \frac{d^2 V}{dz^2}$$

$$V = V^+ e^{-\gamma z} + V^- e^{+\gamma z}$$

$$= \frac{1}{Z} \left( -\cancel{e^{-\gamma z}} \gamma V^+ e^{-\gamma z} + \gamma V^- e^{+\gamma z} \right)$$

$$\gamma V^+ e^{-\gamma z} + \gamma V^- e^{+\gamma z}$$

$$= \gamma \frac{1}{Z} \left[ V^+ e^{-\gamma z} - V^- e^{+\gamma z} \right]$$

$$\gamma = \sqrt{Z Y}$$

$$\frac{V}{Z} \quad \frac{\gamma}{Z} = \frac{\sqrt{Z Y}}{Z}$$

$$= \sqrt{\frac{Y}{Z}}$$

$$= \sqrt{\frac{G + j\omega C}{R + j\omega L}}$$

$$I = \sqrt{\frac{G + j\omega C}{R + j\omega L}} [V_+ e^{-\gamma z} - V_- e^{\gamma z}]$$

$$= \frac{1}{\sqrt{\frac{R + j\omega L}{G + j\omega C}}} \left[ V_+ e^{-\gamma z} - V_- e^{\gamma z} \right]$$

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

For lossless line  $R = 0, G = 0$ .

$$Z_0 = \sqrt{\frac{L}{C}}$$

At  $\mu$ -wave frequency

$\omega L, \omega C$

$$R \ll \omega L,$$

$$G \ll \omega C$$

Propagation constant

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$= (R + j\omega L)^{1/2} (G + j\omega C)^{1/2}$$

$$= \sqrt{j\omega L} \times \sqrt{\frac{R + j\omega L}{j\omega L}} \times \sqrt{j\omega C} \times \sqrt{\frac{G + j\omega C}{j\omega C}}$$



A Using binomial  
 $(1+0.000001)^2$  approximation, we  
 get

$$\sqrt{j\omega L} \left( \frac{R}{2j\omega L} + 1 \right) \sqrt{j\omega C} \left( \frac{G}{2j\omega C} + 1 \right)$$

$$= \sqrt{j\omega L} \sqrt{j\omega C} \left( 1 + \frac{R}{2j\omega L} + \right.$$

$$\left. 1 + \frac{G}{2j\omega C} \right)$$

$$= j\omega \sqrt{LC} \left( 1 + \frac{R}{2j\omega L} + \frac{G}{2j\omega C} \right)$$

$$\frac{1}{2} \left[ R \sqrt{\frac{C}{L}} + G \sqrt{\frac{L}{C}} \right] + j\omega \sqrt{LC}$$

$$= \alpha + j\beta$$

Calculate characteristic  
~~impedance~~ impedance at  
 high frequency  
 frequency

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$= \sqrt{\frac{C}{L}} \sqrt{\frac{R/j\omega L + 1}{G/j\omega C + 1}} = \sqrt{\frac{L}{C}} \sqrt{\frac{\frac{R}{j\omega L} + 1}{\frac{G}{j\omega C} + 1}}$$

$$Z = \sqrt{\frac{L}{C}} \sqrt{\frac{R/j\omega L + 1}{G/j\omega C + 1}}$$

$$Z = \sqrt{\frac{L}{C}}$$

$$\left[ \because \frac{R}{j\omega L} \approx 0 \right. \\ \left. \& \right.$$

$$\left. \frac{G}{j\omega C} \approx 0 \right.$$

since  $\omega$  is very high]

$\omega$   
Rate of change  
of phase  
w.r.to direction

$$V = v(z, t) =$$

$$v(z, t) = R_e \operatorname{Re} | V e^{j\omega t} |$$

$$e^{j\omega t} = \cos(\omega t - \beta z)$$

$$\omega t - \beta z = \text{constant}$$

Phase ~~velocity~~ velocity

$$v_p = \frac{dz}{dt} = \frac{\omega}{\beta}$$

$$\beta = \omega \sqrt{LC}$$

$$v_p = \frac{\omega}{\beta} = \frac{\omega}{\omega \sqrt{LC}} = \frac{1}{\sqrt{LC}}$$

$$\omega - \beta \frac{dz}{dt} = 0 \rightarrow v_p = \frac{\omega}{\beta}$$