

FPGA & Reconfigurable Computing Lecture-6

By

Dr. Swagata Mandal

***Assistant Professor, Electronics and Communication
Jalpaiguri Government Engineering College***

Node Manipulation

- The goal of the BDD is to generate an optimized boolean network with either a less amount of gates or the lowest depth of the gates.
- A given number of transformations can be applied to the network for this purpose
 - **Decomposition:** The decomposition takes a single Boolean function and replaces it with a collection of new expressions.
 - We say that a Boolean function $f(X)$ is decomposable if we can find a function $g(X)$ such that $f(X) = f'(g(X), X)$.
 - Example: The function $f = a\bar{b}\bar{c} + a\bar{b}d + \bar{a}c\bar{d} + bc\bar{d}$ for example operates on 12 literals. Using decomposition, f can be written as: $f = a\bar{b}(\bar{c} + d) + (\bar{a} + b)c\bar{d} = a\bar{b}(\bar{c} + d) + \overline{a\bar{b}}(\overline{\bar{c} + d}) = XY + \overline{X}\overline{Y}$ with $X = a\bar{b}$ and $Y = \bar{c} + d$. This decomposition reduces f to only 8 literals.

Node Manipulation(cont'd)

- **Extraction:** The extraction is used to identify common intermediate sub-functions of a set of given functions in order to avoid redundancy.
- Example: $f = (a + bc)d + e$ and $g = (a + bc)\bar{e}$ can be rewritten as $f = xd + e$ and $g = x\bar{e}$ with $x = a + bc$. The output x of the common part of the circuit will be used as common input for f and g .
- **Factoring:** Factoring is the transformation of SOP-expressions in factored form. For example the function $f = ac + ad + bc + bd + e$ can be rewritten as $f = (a + b)(c + d) + e$
- **Substitution:** Substitution replace an expression e within a function f with the value of an equivalent function $g(X) = e$. For example the function $f = (a + bc)(d + e)$ can be rewritten as $f = g(d + e)$, with $g = a + bc$
- **Collapsing:** Also called **elimination**, collapsing is the reverse operation of the substitution. Collapsing is used to eliminate levels in order to meet the timing constraints. The function $ga + g\bar{b}$ for example will be replaced by $f = ac + ad + b\bar{c}\bar{d}$ with $g = c + d$.

LUT-based Technology Mapping

- The technology independent optimization phase ends with a reduced Boolean network in which the fan-in and fan-out of gates vary.
- The next step consists of allocating LUTs, which are the FPGA library elements for the implementation of the different nodes. Several goals might be followed here.
- If the goal is to minimize the chip area used by the circuit, then the mapping will try to allocate the less possible amount of LUTs.
- If the goal is to minimize the delay of the final circuit, then the mapping will try to minimize the depth of the LUTs used.
- Other goals like testability and low power might also be followed.
- Several LUT technology mapping algorithms have been developed in the past. Depending on their optimization goals, those algorithms can be classified in three categories

LUT-based Technology Mapping(cont'd)

- The first category contains the algorithms, whose goal is to minimize the area.
- This category includes *Chortle-crf*, *MIS-fpga* and the *Xmap*. Due to its popularity and the proof of area optimality for LUTs with less than 5 inputs, we will discuss the *Chortle* algorithm.
- The algorithms in the second category target the delay minimization. Algorithms in this category include *FlowMap*, *Chortle-d*, *DAG-map* and the *MIS-pga-delay*.
- The third category contains algorithms which focus on maximizing the routability. This category includes the Bhat and Hill work as well as the Schlag, Kong and Chang approach.
- Problem Definition: *Given a Boolean network representing a function f and an integer k . Find an implementation of f using only k -inputs LUTs, such that the amount of LUTs use is minimal or the delay of the resulting circuit is minimal*

LUT-based Technology Mapping(cont'd)

- The LUT-based technology mapping is the problem of covering a given graph (the Boolean network) with a set of k -input LUTs.
- The area of the final implementation is defined through the amount of LUT used, the first condition is equivalent to having a covering with a minimal amount of LUTs.
- The delay in an FPGA is influenced by two main factors: The delay in LUTs and the interconnection delay.
- While the delay in LUT is known, the interconnection delay can only be accurately known after the place and route phase.
- Delay estimation at this stage is done using the depth of LUTs in the design, thus assuming the interconnection delay to be one for each wire.
- The more LUTs are available on a path from the input to the outputs the higher the delay in the circuit.

Boolean Network

- *Given a boolean network G , we define the following:*
 - A **primary input (PI)** node is a node without any predecessor.
 - A **primary output (PO)** node is a node without any successor.
 - The level($l(v)$) of a node v is the length of the longest path from the primary inputs to v .
 - The **depth of a network** G is the largest level of a node in G .
 - The fan-in of a node v is the set of gates whose outputs are inputs of v .
 - The fan-out of v is the set of gates that use the output of v as input.
 - Given a node $v \in G$, $input(v)$ is defined as the set of node of G , which are fan-in of v , i.e. the set of predecessors of v .
- *A tree or fan-out-free circuit is one in which each node has a maximal fan-out of one.*
- *A leaf-DAG is a combinational circuit in which the only gates with a fan-in greater than one are the primary inputs.*

K-Bounded network

- **K-Bounded network:** Given a Boolean network G and a subgraph H of G
 - With $input(H)$, we denote the set of all nodes not included in H , which are predecessors of some nodes in H .
 - G is K -bounded if $|input(v)| \leq K$ for all nodes of G .
- A K -bounded Boolean network can be directly mapped to a set of k -inputs LUT by assigning a LUT for each node. However this straightforward approach may not produce the expected optimal results.

Cone at a node: Given a Boolean network G

- A cone at a node v is the tree with root v which spans from v to its primary inputs.
- The cone is K -feasible if:
- Any path connecting two nodes in to v lies entirely in

 


Figure: Example of a K -feasible cone at a node v

K-Bounded network(cont'd)

- With the previous definition of K -feasible cones, the LUT technology mapping becomes the problem of covering the graph with a set of K -feasible cones that are allowed to overlap.
- The technology mapping results in a new DAG in which nodes are K -feasible cones and edges represent communication among the cones.

- Figure shows the covering of a graph with 3-feasible cones and the resulting LUT-mapping to 3-input LUTs.

 
 


Figure : Example of a graph covering with K-feasible cone and the corresponding covering with LUTs

Chortle Algorithm

- The *chortle* algorithm was developed by Francis *et. al* at the University of Toronto in 1991 with the aim of minimizing the amount of LUTs in the implementation of a given circuit.
- It operates in two steps: In the first step, the original Boolean network is partitioned into a forest of trees that are then separately mapped into circuits of K-input LUTs.
- The second step assembles the circuits implementing the trees to produce the final circuit.
- The transformation of the original network into a forest is done by partitioning each fan-out node v .
- Therefore, sub-network rooted at v is duplicated for each input triggered by the fan-out nodes of v .
- The resulting sub-networks are either trees or leaf-DAGs.

Mapping the trees


- The strategy used by *Chortle* to map a tree is a combination of bin packing and dynamic programming.
- In the bin packing problem, items of different volumes must be packed into a finite number of bins or containers each of volume V in a way that minimizes the number of bins used.
- Each tree is traversed from the primary inputs to the primary outputs.
- At each node v , a circuit referred to as the ***best Circuit***, implementing the cone at v extending from the node to the primary inputs of the network is constructed.
- The ***best circuit*** is characterized by two main factors: The tree rooted at v and represented by a cone must contain the minimum number of LUTs and the output LUT (the root-LUT) implementing v should contain the maximum number of unused input pins.

Mapping the trees(cont'd)


- For a primary input p the *best circuit* is a single LUT whose function is a buffer.
- Using the dynamic programming, the *best circuit* at a node v can be constructed from its fan-in nodes, because each of them is already optimally implemented.
- The procedure enforces the use of the minimum number of LUTs at a given node.
- The *best circuit* is then constructed from the minimum number of LUTs used to implement its fan-in nodes.
- The secondary goal is to minimize the number of unused inputs of the circuit rooted at node v .
- The construction of the tree is done in two steps. First a *two-level decomposition* of the cone at v is constructed and then this decomposition is converted into a *multi-level decomposition*.

Two-level decomposition

 - The two-level decomposition consists of a single first level node and several two-level nodes.
- Each second level node implements the operation of the node being decomposed over a subset of the fan-in LUTs.
- The first level node is not implemented at this stage. This will be done in the second phase of the algorithm where the two-level representation is converted into a multi-



(a) Fan-in LUTs at a node

 

(b) The two-level decomposition

Fig: Chortle two-level decomposition

Two-level decomposition(cont'd)

- The two-level decomposition is constructed using a bin packing algorithm approach.
- In the traditional bin packing algorithm, the goal is to find the minimum number of bins with a given capacity, into which a set of boxes can be packed.
- In the *Chortle* algorithm, the bins are the second-level LUTs and the boxes are the fan-in LUTs.
- The capacity of each bin is the number k of LUT inputs.
- The packing at this stage consist of combining two fan-in LUTs, LUT1 that realizes the function f_1 and LUT2 that realizes the function f_2 into a new LUT (suppose LUT_r) that implements the function $f_1 \oslash f_2$, where \oslash is the operation implemented by the fan-out node.

Two-level decomposition(cont'd)

- In the previous figure (a) shows an original graph and its decomposition is shown in figure (b).
- In example, the \oplus is the OR function. The pseudo code of the two-level decomposition algorithm is given in below
- Chortle's two-level decomposition

Start with an empty list of LUTs

While there are unpacked fan-in LUTs **do**

If the largest unpacked fan-in LUT will not fit within any LUT in the list **then**
 create an empty LUT and add it to the end of the list

End if


 pack the largest unpacked fan-in LUT into the first LUT it will fit within

End while

Two-level decomposition(cont'd)

- This algorithm uses a *First-Fit-Decreasing (FFD)* method
- The FFD algorithm packs each number in order of non-increasing size into the first bin in which it fits, which places a fan-in LUT to be packed into the first LUT it will fit within.
- However, a *Best-Fit (BF)* approach that packed the fan-in LUTs into the LUT they best fit in, can also be used.
- **Multi-level Decomposition:** In the second step, the first-level nodes are implemented using a tree of LUTs.
- The number of LUTs used is minimized by using second level LUTs that have unused pins to implement a portion of the first-level three as shown in Figure

Multi-level Decomposition

 

Example of multi-level decomposition

Multi-level

Decomposition(cont'd)

- The detailed procedure for converting two-level decomposition into a multi-level decomposition is given in algorithm
- Chortle's multi-level decomposition
- **while** there is more than one unconnected LUT **do**
- **if** there are no free inputs among the remaining unconnected LUTs **then**
- create an empty LUT and add it to the end of the LUT list
- **end if**
- connect the most filled unconnected LUT to the next unconnected LUT with a free input
- **end while**
-

Thank You